









[Fig. 15-25] "new class A" circuit

[Fig. 15-25] shows the entire circuit used in the new class A amplifier; the block enclosed by the dotted line is the synchro-bias circuit which is the key to the success of this revolutionary configuration.